Amendments to the Drawings

Please replace the drawings previously on file with new drawings submitted herewith.

Fig. 1

$629 =$

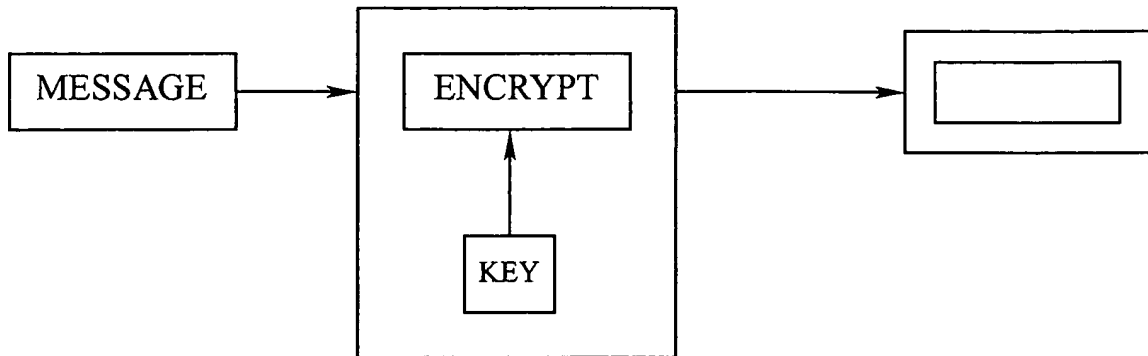| 2^9	2^8	2^7	$+2^6)$	$+2^5$	$+2^4$		$+2^2$		$+2^0$
1	0	0	1	1	1	0	1	0	1
+1	+1	+1	−1	+1	+1	+1	−1	+1	−1
2^9	$+(2^8$	-2^7	$-2^6)$	$+2^5$	$+2^4$	$+(2^3$	$-2^2)$	$+(2^1$	$-2^0)$

$628 =$

2^9			$+2^6)$	$+2^5$	$+2^4$		$+2^2$		
1	0	0	1	1	1	0	1	0	0
+1	+1	+1	−1	+1	+1	+1	−1	+1	−1
									−1
2^9	$+(2^8$	-2^7	$-2^6)$	$+2^5$	$+2^4$	$+(2^3$	$-2^2)$	$+(2^1$	$-2^0)$

Fig. 2

LSB . . . . MSB

$$\boxed{b_0}\ \boxed{b_1}\ \boxed{b_2}\ \Big)\ \boxed{b_{n-1}}\ \boxed{b_n}$$

IF $b_i = 1$
THEN $Q \leftarrow 2Q + P$

START   H0   IF $i < 0$ DONE

IF $b_i = 1$
THEN
$Q \leftarrow 2Q - P$

IF $b_i = 0$
THEN
$Q \leftarrow 2Q + P$

30

H1

IF $i = 0$ THEN $Q \leftarrow Q - P$

IF $b_i = 0$
THEN $Q \leftarrow 2Q - P$

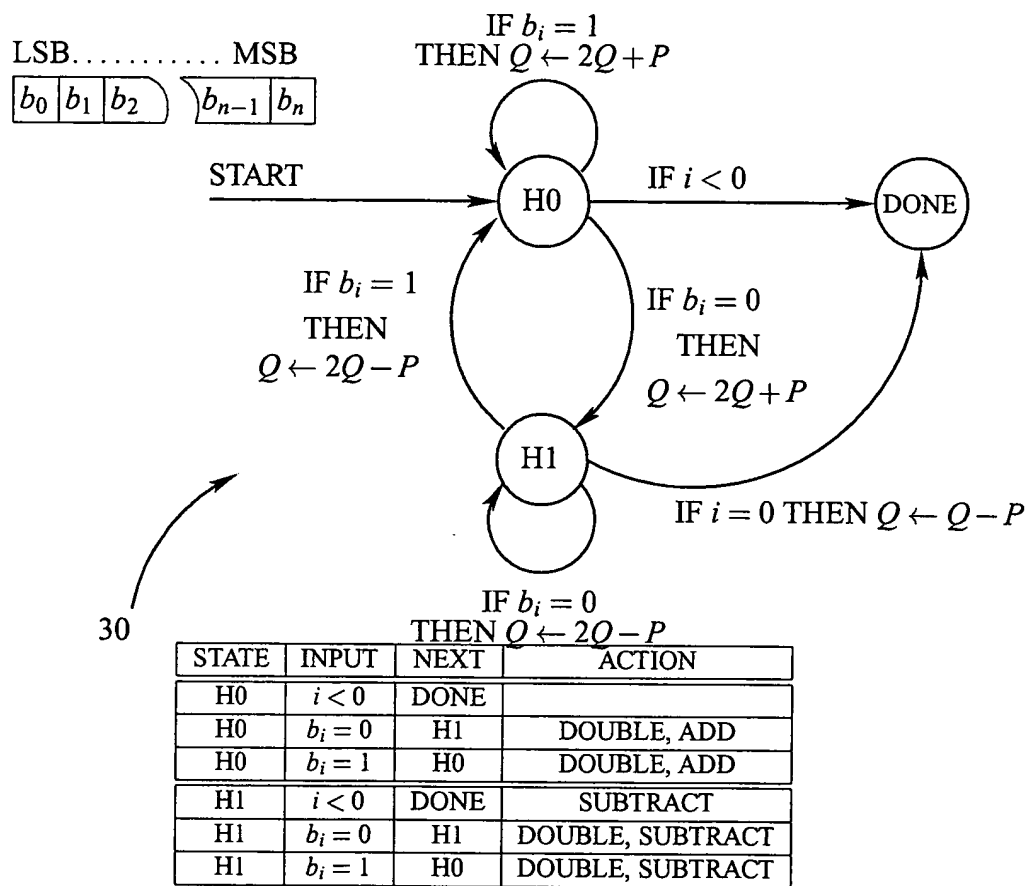| STATE	INPUT	NEXT	ACTION
H0	$i < 0$	DONE	
H0	$b_i = 0$	H1	DOUBLE, ADD
H0	$b_i = 1$	H0	DOUBLE, ADD
H1	$i < 0$	DONE	SUBTRACT
H1	$b_i = 0$	H1	DOUBLE, SUBTRACT
H1	$b_i = 1$	H0	DOUBLE, SUBTRACT

Fig. 3

```
BEGIN:
    i := N                ; START FROM MSB                          L1
    Q := 0                ; INITIALIZE ACCUMULATOR                  L2
    H := 0                ; INTIALIZE STATE                         L3

LOOP:                     ; FOR ALL BITS
    Q := Q + Q            ; DOUBLE ACCUMULATOR                      L4
    IF H = 0             ; IF H STATE IS SET                        L5
      Q := Q + P          ;   ADD BASE POINT TO ACCUMULATOR         L6
      GOTO ENDLOOP        ;                                         L7
    ELSE                  ; ELSE
      Q := Q - P          ;   SUBTRACT BASE POINT                   L8
      GOTO ENDLOOP        ;                                         L9

ENDLOOP:
    H := b[i]             ; SET H STATE TO COMPLEMENT OF b[i]       L10
    i := i - 1            ; PROCESS NEXT BIT                        L11
    IF i ≥ 0             ; IF BIT EXISTS                            L12
      GOTO LOOP           ;   CONTINUE AT TOP OF LOOP               L13
    IF H = 0             ; IF EXITING FROM H = 0 STATE              L14
      Q := Q + (−P)       ;   CORRECT RESULT BY FINAL SUBTRACT      L15
    END                                                            L16
```
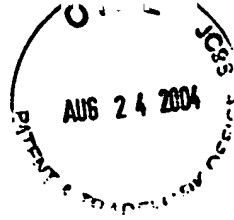
Fig. 4

```
BEGIN:
    i := N              ; START FROM MSB                          LL1
    Q := 0              ; INITIALIZE ACCUMULATOR                  LL2

H0:                     ; STATE ENTRY POINT
    Q := Q + Q          ; DOUBLE ACCUMULATOR                      LL3
    Q := Q + P          ; ADD BASE POINT TO ACCUMULATOR           LL4
    GOTO ENDLOOP        ; BRANCH TO END OF LOOP TESTS             LL5

H1:                     ; STATE ENTRY POINT
    Q := Q + Q          ; DOUBLE ACCUMULATOR                      LL6
    Q := Q + (-P)       ; SUBTRACT BASE POINT FROM ACCUMULATOR    LL7
    GOTO ENDLOOP        ; BRANCH TO END OF LOOP TESTS             LL8

ENDLOOP:                ; END OF LOOP TESTS
    IF b[i] = 1         ; IF CURRENT BIT IS SET                   LL9
       GOTO NEXT H0     ;   FOLLOW H0 PATH                        LL10
                        ; ELSE FALL INTO H1 PATH
NEXT H1:                ; H1 PATH
    i := i - 1          ; PROCESS NEXT BIT                        LL11
    IF i > 0            ; IF BIT EXISTS                           LL12
       GOTO H1          ;   EXECUTE H1 STATE                      LL13
    Q := Q + (-P)       ; ELSE CORRECT RESULT AND END             LL14
    END                                                          LL15

NEXT H0:                ; H0 PATH
    i := i - 1          ; PROCESS NEXT BIT                        LL16
    IF i > 0            ; IF BIT EXISTS                           LL17
       GOTO H0          ;   EXECUTE H0 STATE                      LL18
    END                 ; ELSE END                                LL15
```

Fig. 5

BEGIN:
$i := N$
$Q := 1$

H0:
$Q := Q \cdot Q \ (Q^2)$
$Q := Q \cdot M$
GOTO ENDLOOP

H1:
$Q := Q \cdot Q$
$Q := Q/M \ (Q \cdot M^{-1})$

60 ENDLOOP:
IF $b[i] = 1$ GOTO ENDLOOP

NEXT H1:
$i := i - 1$
IF $i > 0$
GOTO H1
$Q := Q/M$
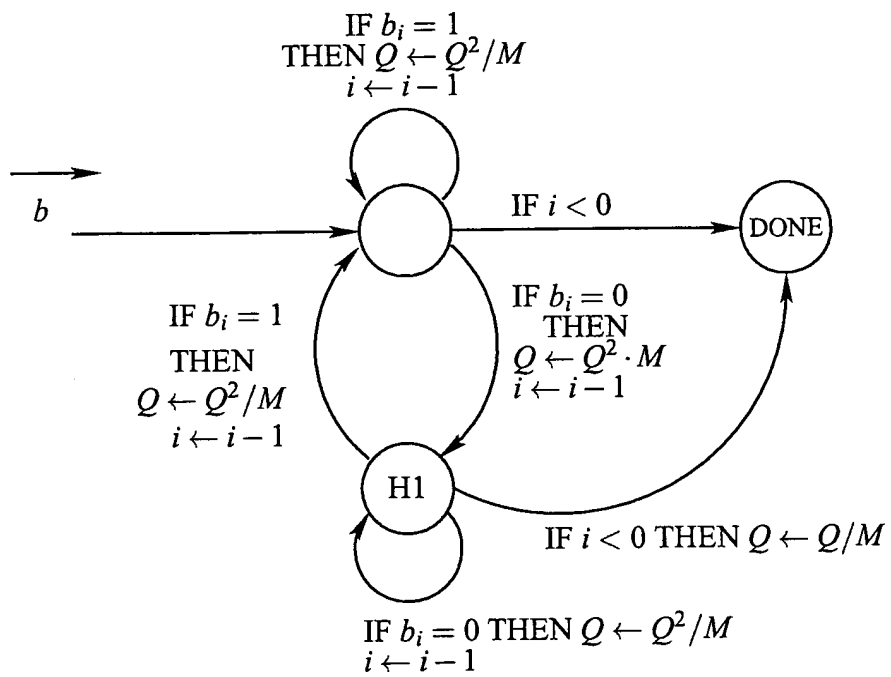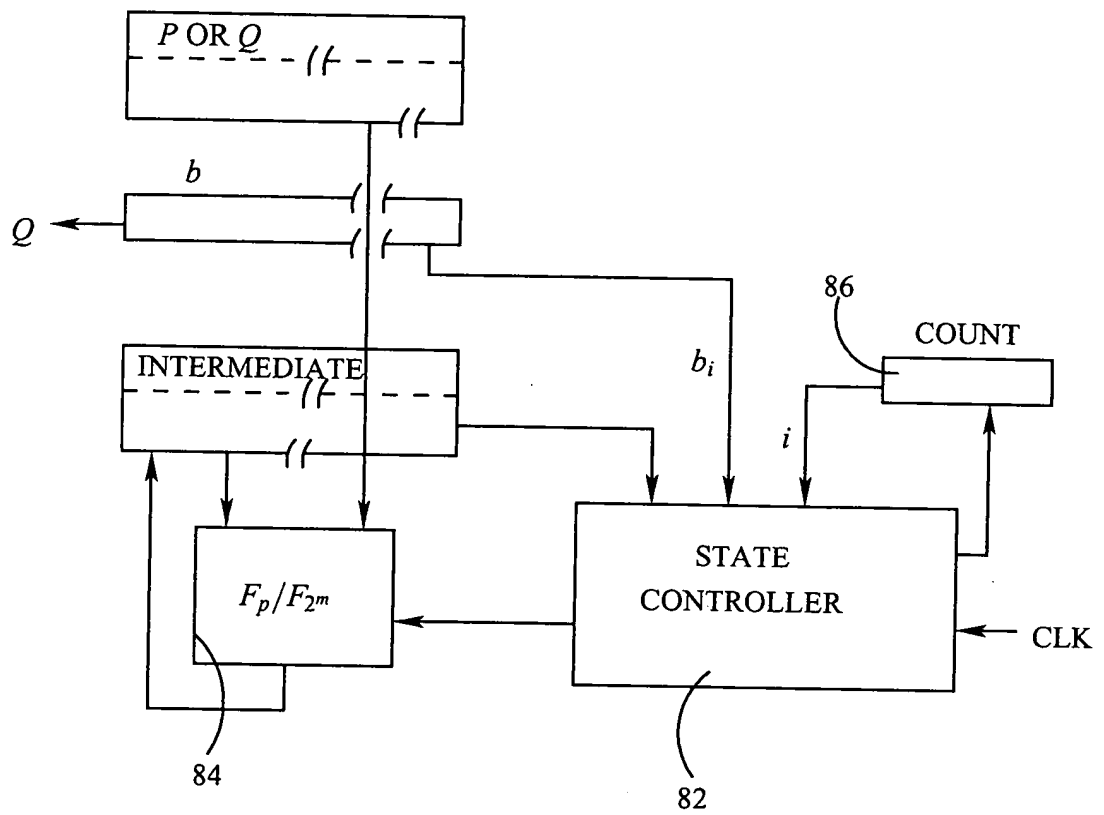END

NEXT H0:
$i := i - 1$
IF $i > 0$
GOTO H0
END

Fig. 6

IF $b_i = 1$
THEN $Q \leftarrow Q^2/M$
$i \leftarrow i - 1$

b

IF $i < 0$

DONE

IF $b_i = 1$

THEN

$Q \leftarrow Q^2/M$
$i \leftarrow i - 1$

IF $b_i = 0$
THEN
$Q \leftarrow Q^2 \cdot M$
$i \leftarrow i - 1$

H1

IF $i < 0$ THEN $Q \leftarrow Q/M$

IF $b_i = 0$ THEN $Q \leftarrow Q^2/M$
$i \leftarrow i - 1$

Fig. 7

P OR Q

b

Q

INTERMEDIATE

b_i

86

COUNT

i

F_p/F_{2^m}

STATE
CONTROLLER

CLK

84

82

Fig. 8